



### EE431 Quiz No. 3:

Date: Thursday, November 29, 2001

Time = 40 minutes

Texts and Notes allowed

1. Generate a schematic diagram for the Verilog descriptions given below.  
For the flip/flops in your schematic, use a D type with clock enable, asynchronous set and asynchronous clear.

- (1) (a) 

```
module circuit_1 (clk, a, b, c, Q)
    input clk, a, b, c;
    output Q;
    reg Q;
    always @ (posedge clk)
    begin
        if (a == 1'b1) Q <= 1'b1
        else if (b == 1'b1) Q <= c;
        else Q <= c ^ Q;
    end
```
- (1) (b) 

```
module circuit_2 (clk, a, b, c, d, r)
    input clk, a, b, r;
    input [1:0] c;
    output d;
    reg Q1, Q2, d;
    always @ (posedge clk or negedge r)
    if (r == 1'b0) begin Q1 <= 1'b0; Q2 <= 1'b0; end
    else
    if ( a == b)
        case (c)
            2'b00: begin Q1 <= c[1];    Q2 <= Q1; end
            2'b01: begin Q1 <= d ^ Q2; Q2 <= b; end
            2'b10: begin Q1 <= d;      Q2 <= Q1; end
            2'b11: begin Q1 <= d;      Q2 <= Q1; end
        endcase
    else begin Q1 <= 1'b0; Q2 <= 1'b1; end
```

```

always @ (Q1 or Q2 or d)
if (a == Q2) d = Q1;
else if (Q1 == Q2) d = Q2;
else d = b;

```

```

endmodule

```

2. Consider the structural description below

```

module circuit_3(clk, y)
input clk;
output y
wire x, d;
DFFE flop_1 (.clk(clk), .d(d), .Q(x));
DFFE flop_2 (.clk(clk), .d(x), .Q(y));
nor nor_1(d,x,y);
endmodule

```

DESCRIPTION OF CONNECTION LIST FOR D FLOP

```

DFFE instance_name (
.D(d),          // the d input
.CLK(clk),      // the clock, positive edge trigger
.ENA(enable),   // if used, D goes to Q on clock edge when
                // ENA is high otherwise Q does not change
.CLRN(clear_bar), // if used, clears Q when low
.PRN(set_bar),   // if used, sets Q when low
.Q(q)           // output
);

```

- (1) (a) Write a behavioral description in Verilog of the circuit described above. For this description use only blocking equalities in the "always" constructs.

- (1) (b) Write a behavioral description in Verilog of the circuit described above. For this description use only non-blocking equalities in the "always" constructs.

3. Consider the structural description below

```
module circuit_4(clk_1, clk_2, y)
input clk_1, clk_2;
output y
wire x, w;
DFFE flop_1 (.CLK(clk_1), .D(1'b1), .CLR(y), .Q(x));
DFFE flop_2 (.CLK(clk_2), .D(1'b1), .CLR(y), .Q(w));
nand nand_1 (y,w,x);
endmodule
```

- (1) (a) Write a behavioral description in Verilog of the circuit described above. For this description use only blocking equalities in the "always" constructs.
- (1) (b) Write a behavioral description in Verilog of the circuit described above. For this description use only non-blocking equalities in the "always" constructs.